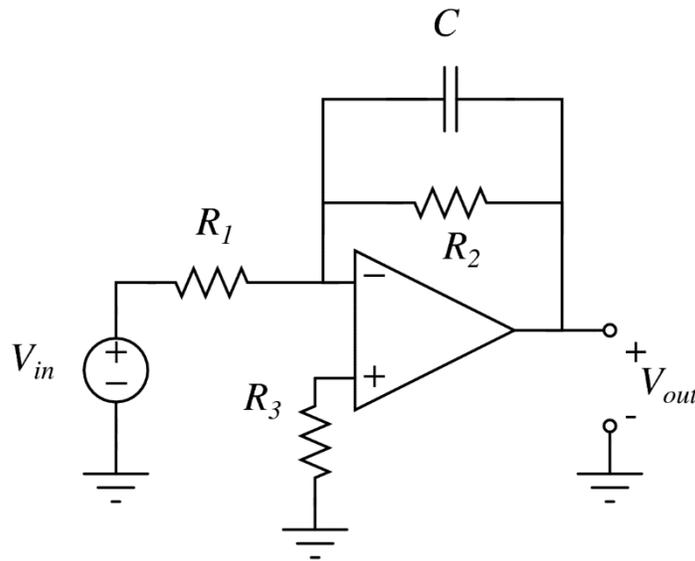


Problem Set 2
Due: Thursday September 26, 2013

Please show all work throughout. You will lose credit if you do not.

Problem 1: Basic op-amp circuit analysis

You are given the following circuit:




Please answer the following questions about this circuit, assuming that the source v_{in} is sinusoidal.

- At low frequency, does a capacitor appear as a short or as an open? Explain using both equations and words. Using this knowledge, sketch an equivalent low-frequency circuit model.
- What is the gain of the circuit that you drew in part a? You must show your work in order to receive credit.
- At high frequency, does a capacitor appear as a short or as an open? Explain using both equations and words. Using this knowledge, sketch an equivalent high-frequency circuit model.
- What is the gain of the circuit that you drew in part c? You must show your work in order to receive credit.
- What is the gain of the complete circuit at any given frequency ω ? Show that this result is consistent with your intuitive results from parts b and d by taking the limit of this expression as $\omega \rightarrow 0$ and as $\omega \rightarrow +\infty$.

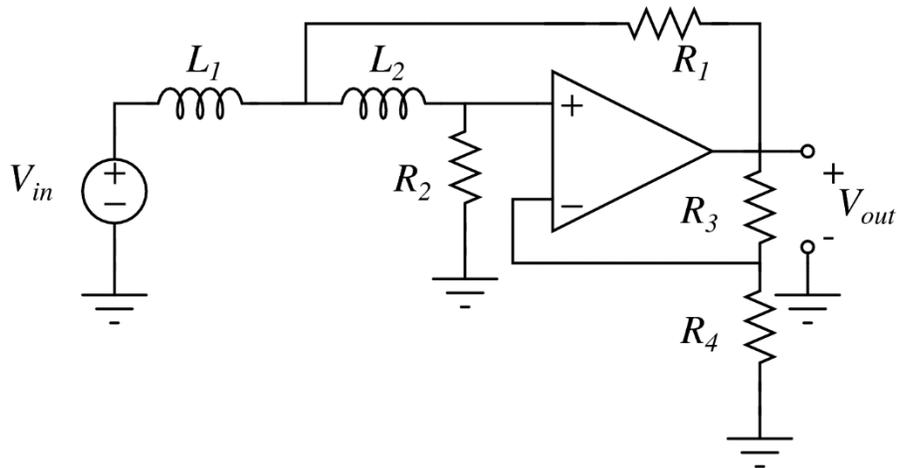Problem 2: Basic Op-Amp Circuit Analysis


Please answer the following questions about this circuit, assuming that the source v_{in} is sinusoidal.



- What is the gain from V_{in} to V_{out} ?
- Is this a low-pass or high-pass filter? Explain carefully using your transfer function from part a.
- Does this circuit provide gain or attenuation at DC? Explain carefully using your transfer function from part a.

Problem 3: Basic Op-Amp Circuit Analysis

You are given the following circuit:

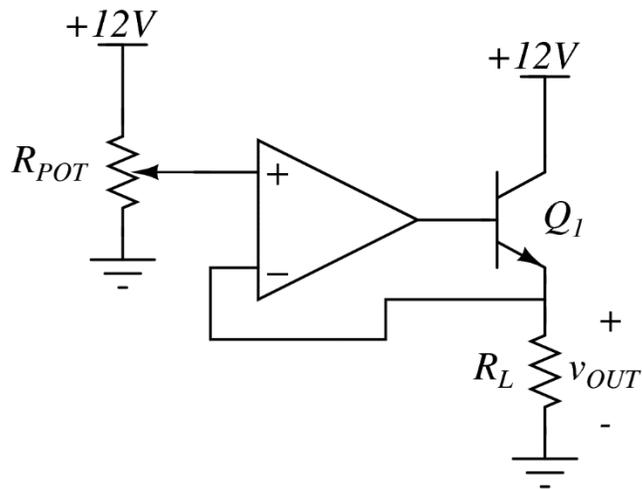

If the potentiometer is set to 50%, what is the value of the output voltage? You must show your work.